

# EXAMINATION : AUTHORISATION B

April 2016

Practical Test

Time Allowed - 1Hr

Name & Surname \_\_\_\_\_  
(In Block letters)

Index No. \_\_\_\_\_

---

The electrical load of a small factory consists of the following components.

- a. Two - 10KW three phase motors with power factor 0.8 and an efficiency of 85%.
- b. One - 40KW three-phase machine having a power factor of 0.85 and an efficiency of 78%.
- c. Four - 3KW, thermostatically controlled water heaters.
- d. Eight - 32A ring circuits feeding 13 A socket outlets.
- e. 15KW of discharge lighting with power factor corrected to 0.85.
- f. Fifty lighting points for filament lamps.

The power supply is three phase 415/240 volts.

- i. Draw a single line diagram of the main switch-board indicating the current rating of each switch and type of protection.
- ii. Calculate the total current demand.
- iii. Taking a diversity factor of 80 per cent and allowing a total of 50A for future expansion calculate a suitable size of switch-board and main circuit breaker for the installation.

Show all calculations.

(Total 40 Marks)