
EXAMINATION: AUTHORISATION A

September 2018

Practical Test			Time Allowed - 1Hr				
Name & Surname Index No							
The	attache	d drawings show the building plan for an apartm	ent. The electrical installation is	to be supplie			
from	a 230	V, 50Hz single-phase supply. The distribution sup	plying the electrical installation is	marked on th			
build	ling pla	ns.					
a.	On th	e building plans provided design the electrical ins	tallation for the apartment. In your	design besid			
	the lighting points and power circuits include a water heater circuit rated at 2500W and an air condition						
	circui	it for the sitting room rated at 3000W.					
	i.	Mark the lighting circuits on one building plan a	and the power circuits on a separate	building plan			
	ii.	In addition state how many circuits do you s	uggest for this electrical installati	ion and clear			
		specify the area (rooms) that each circuit will be	•				
	iii.	Indicate on the attached drawings, the propose	d circuits and conduit routes for the				
		power circuits from the distribution board.		(20 marks)			
b.	Draw	a suitable Consumer Unit Layout for the above	e installation showing the MCB's,	Main Switch			
	RCD	and any other protection that may be required for	the installation.	(8 marks)			
c.	List t	he sequence of test that need to be performed befo	re energising the installation	(6 marks)			
d.	Desci	ribe how you would perform an insulation resistan	ce test for this installation.	(6 marks)			

END OF PAPER

	19			
à				

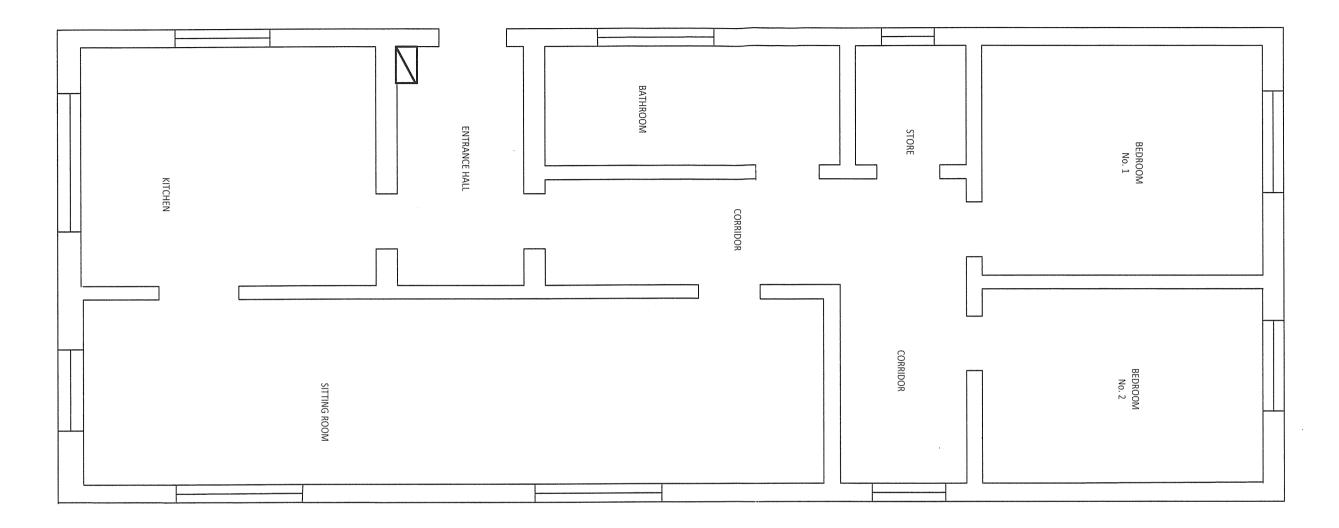

ONE-WAY SWITCH

TWO-GANG SWITCH


TWO- WAY SWITCH

CEALING LUMINAIRE

WALL MOUNT LUMINAIRE

TWIN SWITCHED SOCKET OUTLET

MAIN DISTRIBUTION BOARD

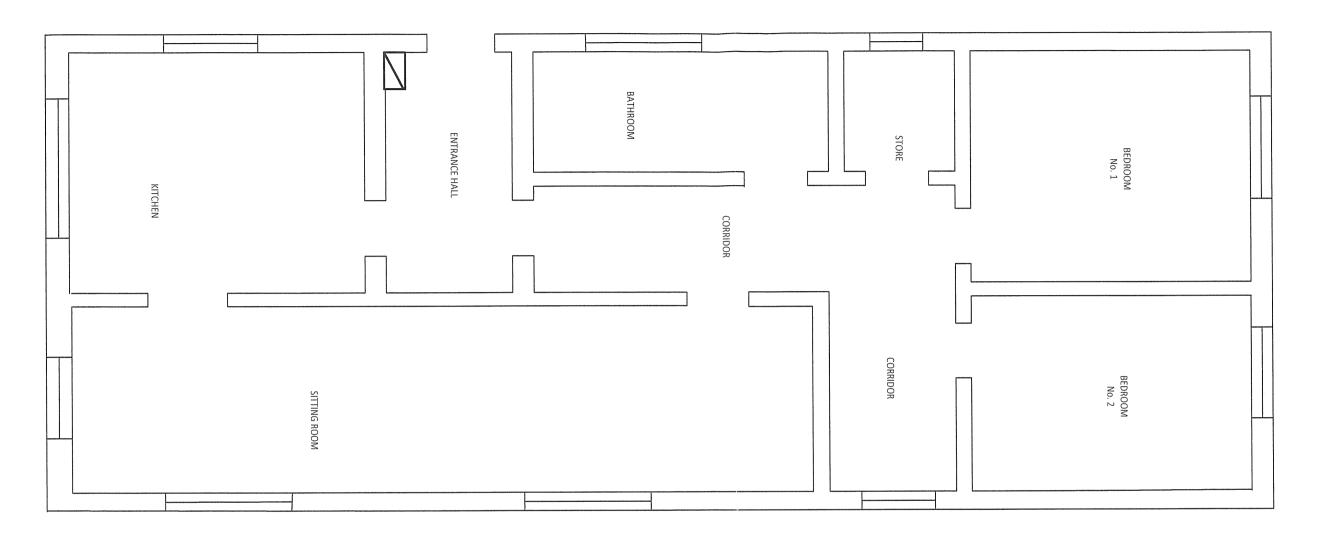

.6	ONE-WAY SWITCH
2	TWO-GANG SWITCH
1	TWO- WAY SWITCH
×	CEALING LUMINAIRE
\rtimes	WALL MOUNT LUMINAIRE
<u></u>	TWIN SWITCHED SOCKET OUTLE
	MAIN DISTRIBUTION BOARD