

**WRITE ALL YOUR WORK IN THE ANSWER BOOK PROVIDED
EVERY ANSWER SHOULD INCLUDE ALL WORKINGS, NECESSARY
DIAGRAMS AND FORMULAE.**

START EACH ANSWER ON A FRESH PAGE.

Answer any FIVE Questions

1. A 6 pole 3-phase delta connected induction motor is connected to a 400V 50Hz supply. The motor operates at lagging power factor of 0.8. This motor is used to drive a goods lift, having total load of 120kg, at a rate of 3.3m/sec. For full load conditions the efficiency of the lift and the motor is 80% and 85% respectively. The slip frequency is 2Hz. Take force of gravity as 9.81N/kg.

For full load conditions calculate:

- a) The output and input power of the motor (6 marks)
- b) The line current drawn from the supply (3 marks)
- c) The current in each winding (2 marks)
- d) The synchronous speed (2 marks)
- e) The rotor speed (4 marks)
- f) The output torque of the motor (3 marks)

- 2a. With lead-acid storage batteries, what are the causes of:

- i. sulphating of plates (2 marks)
- ii. buckling of plates (2 marks)
- iii. disintegration of plates (2 marks)

- b. A battery of cells of total emf 40 volts and total internal resistance 2 ohms is connected in parallel with a second battery of 44 volts and internal resistance 4 ohms. A load resistance of 6 ohms is connected across the ends of the parallel circuit.

- i. draw a neat circuit diagram show all the components and indicate clearly the current directions. (2 marks)
- ii. calculate the current in battery A. (4 marks)
- iii. calculate the current in battery B (4 marks)
- iv. the current in the load resistance and its direction. (4 marks)

- 3a. Draw circuit diagrams of:

- i. A short shunt DC Generator (2 marks)
- ii. A Long Shunt DC Generator (2 marks)
- iii. Draw the curves of the terminal voltage against the current output of a level compound and an over compound DC Generator. (2 marks)

- b. A long shunt generator ($R_a=0.05\text{ohms}$, $R_{se} = 0.06\text{ohms}$, $R_{sh} = 12\text{ohms}$) supplies a load of 98A at a p.d. of 240V. Determine the armature current and the value of the generated EMF. (7 marks)


- c. A short shunt generator ($R_a = 0.1\text{ohm}$, $R_{se} = 0.12\text{ohm}$, $R_{sh} = 240\text{ohms}$) generates a total EMF of 245 Volts when the armature current is 50 A. Determine the terminal voltage for this load. (7 marks)

4. A number of 13A single-phase sockets are wired as a ring circuit and fed from a consumer unit having a supply voltage of 230V 50Hz. The circuit is protected by a 32A MCB.

Three (3) electric heaters are connected to this ring circuit as shown. The resistance of a single conductor is 0.02ohms/100m.

Calculate:

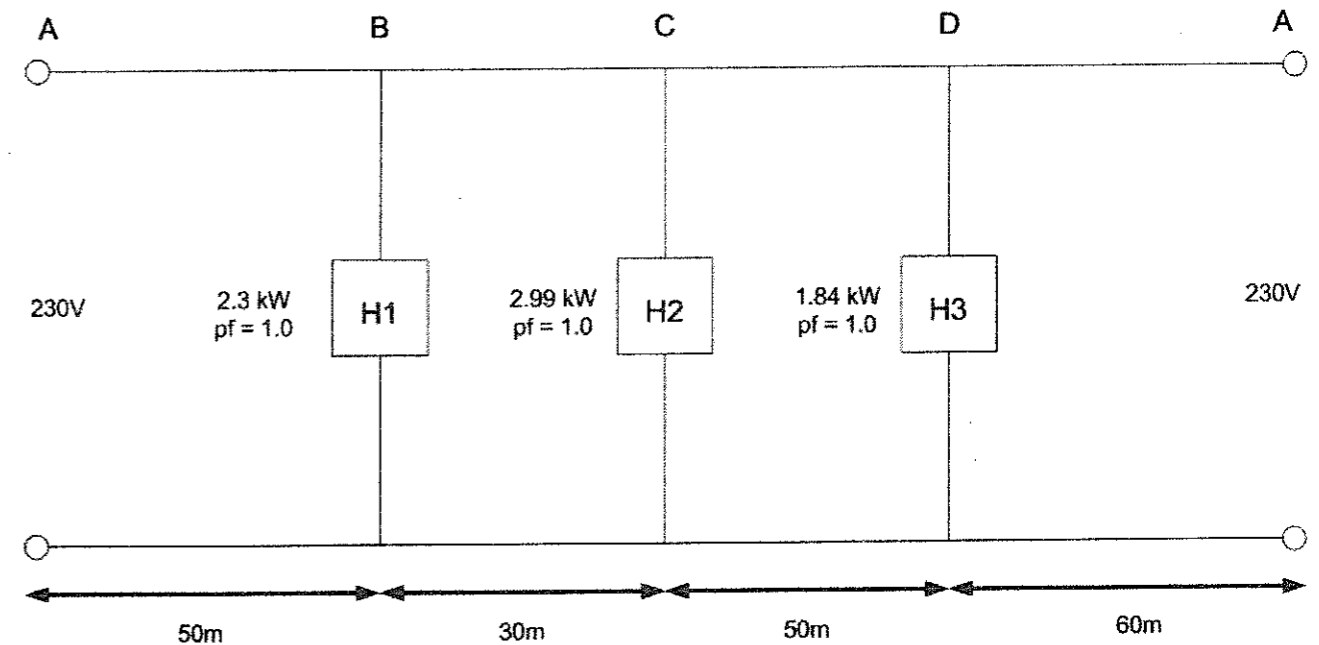- a) The resistance in each branch (4 marks)
- b) The current in each branch (9 marks)
- c) The voltage drop in each branch (4 marks)
- d) The voltage across each load (3 marks)



5. A parallel circuit consists of two branches. Branch A has a pure inductance of 120mH and Branch B has 25μf capacitance, The supply to the circuit is 230V, 50Hz. Determine:

- (a) The Branch currents in A & B. (4 marks)
- (b) The supply current. (3 marks)
- (c) Impedance of the parallel circuit. (2 marks)
- (d) The power consumed. (3 marks)
- (e) Draw the phasor diagram. (4 marks)
- (f) What is the resonant frequency of the parallel circuit. (hint: since R is negligible you can use the series circuit resonant formula). (4 marks)

6. A 20kVA, single-phase double - wound, 50Hz, 400/230Volts step-down transformer gave the following test results:-

Open-circuit test 400Volts applied to primary: power taken 220Watts;

Short-circuit test: power required to circulate full load current in short-circuit secondary 240Watts. Calculate:

- (a) The full load efficiency assume the power factor to be unity. **(5 marks)**
(b) The full load terminal voltage if the transformer having 5% regulation and with an open secondary voltage of 230V **(5 marks)**
(c) If the 20kVA transformer is energized continuously for 15 hours (assume unity power factor), calculate its All-day efficiency, **(5 marks)**
(d) If the double wound transformer is replaced by an auto-transformer, describe the operation and precautions to be taken according to the I.E.E. regulations. **(5 marks)**

END OF PAPER

**EXAMINATION FOR THE ISSUE OF A LICENCE TO ACT AS
WIREMAN - LICENCE 'B'**

June 2012

Paper I (Theory)

Time Allowed: 3 Hrs