PLEASE WRITE YOUR ANSWERS AND DRAWINGS HERE



EXAMINATION: AUTHORISATION A

September 2022

Practical Test

Time Allowed - 11/2 Hr

Name & Surname	Index No
'In Block letters)	

- 1. The diagram below shows a typical installation for a flat. Study the diagram well and then answer the following questions.
 - a. Divide the installation into a suitable number of circuits. Show your design on a suitable schematic drawing which should indicate clearly:
 - i. each accessory clearly numbered
 - ii. all cable sizes
 - iii. Il fuse sizes
 - iv. earthing system
 - v. Consumer Unit Layout.
 - b. If the flat is to be wired with PVC single core cables run in concealed plastic conduit, show on the diagram below the proposed runs of conduit.
 - c. Prepare a detailed Bill of Quantities showing the amount and size of each item of material required to complete the installation.

(Total 40 marks)

t + 356 2598 2958 e myexams@gov.mt | www.myexams.gov.mt

4

